

# RF MIXER SIGNAL CIRCUIT


## Superheterodyne Frequency Converter — BJT 2N2222A

Active mixer with dual LC IF bandpass filter ·  $f_{RF} = 12\text{ MHz}$  ·  $f_{LO} = 20\text{ MHz}$  ·  $f_{IF} = 8\text{ MHz}$

### QUICK SPECIFICATIONS

| Parameter          | Value        |
|--------------------|--------------|
| RF Input Frequency | 12 MHz       |
| LO Frequency       | 20 MHz       |
| IF Output (wanted) | 8 MHz        |
| Sum Product        | 32 MHz       |
| IM3 Lower          | 4 MHz        |
| IM3 Upper          | 28 MHz       |
| Supply Voltage     | 12 V DC      |
| Active Device      | 2N2222A NPN  |
| RF Input Level     | 10 mVrms     |
| LO Drive Level     | 50 mVrms     |
| IF Filter Topology | Dual LC BPF  |
| IF Load ( $R_2$ )  | 1 k $\Omega$ |

### DEVICE / CIRCUIT PHOTOGRAPH

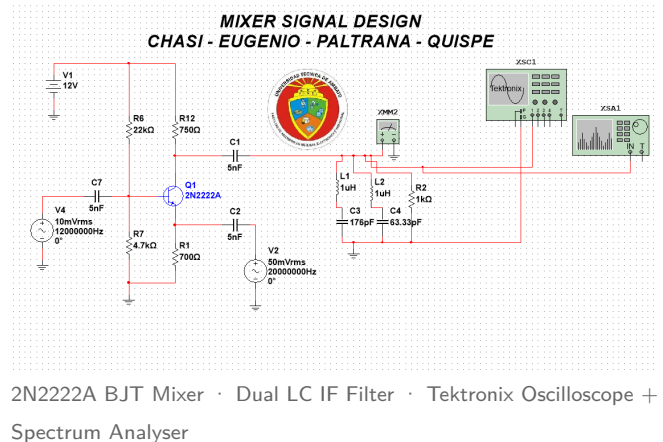

### SIMULATION ENVIRONMENT

**Software:** NI Multisim (EWB)  
**Instruments:** Tektronix oscilloscope (XSC1), Spectrum Analyser (XSA1), Multimeter (XMM2)  
**Topology:** Common-emitter BJT mixer, LO injected at emitter  
**Bias:** Voltage-divider,  $R_6/R_7$

## 1. THEORY OF OPERATION — SUPERHETERODYNE MIXER

A **frequency mixer** performs the nonlinear multiplication of two input signals — the Radio-Frequency (RF) carrier and a Local Oscillator (LO) — generating new spectral components at their sum and difference frequencies. This circuit implements a **single-transistor active mixer** using the NPN BJT 2N2222A biased in the active region, where its collector current exhibits the nonlinear transconductance characteristic that drives the frequency-conversion process.

The RF signal ( $f_{RF} = 12\text{ MHz}$ ,  $V_{RF} = 10\text{ mV}_{\text{rms}}$ ) is applied via coupling capacitor  $C_7$  to the transistor base. The LO signal ( $f_{LO} = 20\text{ MHz}$ ,  $V_{LO} = 50\text{ mV}_{\text{rms}}$ ) is injected at the emitter through  $C_2$ , modulating the device transconductance

at the LO rate. The desired Intermediate Frequency  $f_{IF} = |f_{LO} - f_{RF}| = 8 \text{ MHz}$  is extracted by a two-stage LC bandpass filter ( $L_1, C_3$  and  $L_2, C_4$ ).

### Core Frequency-Conversion Equations

$$\begin{aligned} v_{RF}(t) &= A_{RF} \cos(2\pi f_{RF} t) \\ v_{LO}(t) &= A_{LO} \cos(2\pi f_{LO} t) \end{aligned} \quad \begin{aligned} (1) \quad v_{out}(t) &= v_{RF}(t) \cdot v_{LO}(t) \\ (2) \quad &= \frac{A_{RF} A_{LO}}{2} [\cos(2\pi f_{IF} t) + \cos(2\pi(f_{RF} + f_{LO})t)] \\ (3) \end{aligned}$$

**Product-to-sum trigonometric identity:**

$$\cos(A) \cos(B) = \frac{1}{2} [\cos(A - B) + \cos(A + B)]$$


The  $\frac{1}{2}$  factor represents the inherent **6 dB conversion loss** of an ideal multiplier.  $f_{IF} = |f_{LO} - f_{RF}| = 8 \text{ MHz}$

**General spurious products:**  $f_{spur} = |m \cdot f_{RF} \pm n \cdot f_{LO}|, \quad m, n \in \mathbb{Z}$

## 2. CIRCUIT SCHEMATIC ANALYSIS
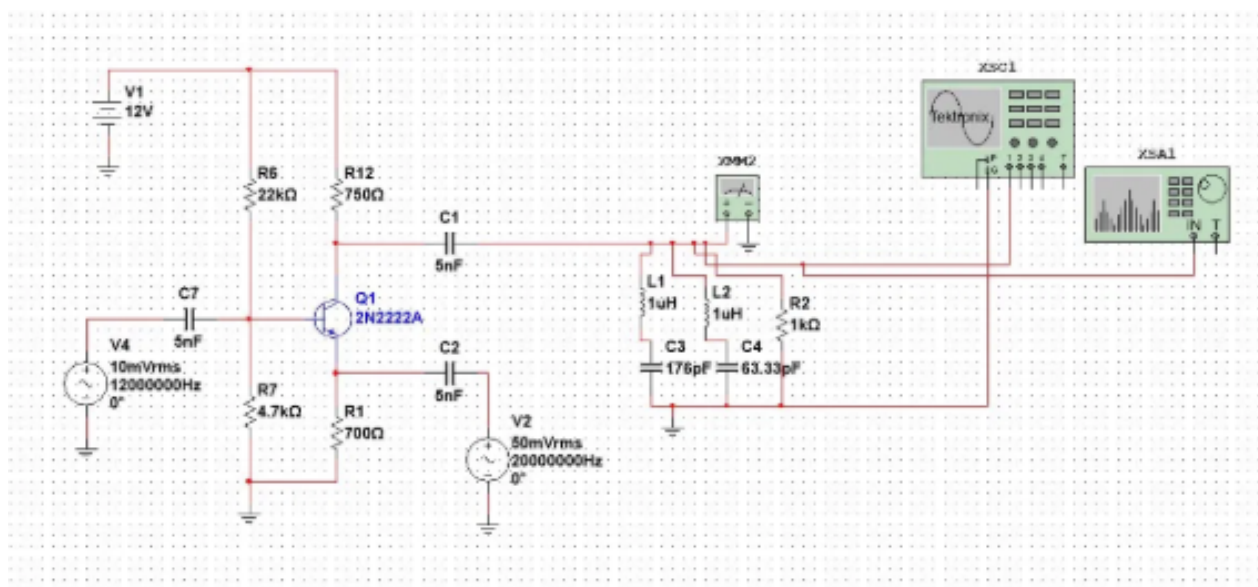
### SIMULATED SCHEMATIC — NI MULTISIM

Images 2–3: Component layout and signal injection points



### Component Inventory & Functional Description

| Ref. | Value             | Function                                              | Stage      |
|------|-------------------|-------------------------------------------------------|------------|
| V1   | 12 V DC           | Supply rail — BJT bias network                        | Bias       |
| V4   | 10 mVrms / 12 MHz | RF input signal source                                | RF Input   |
| V2   | 50 mVrms / 20 MHz | Local oscillator injection at emitter                 | LO Input   |
| Q1   | 2N2222A NPN       | Active mixing device — nonlinear transconductance     | Mixer Core |
| R6   | 22 k $\Omega$     | Upper voltage divider — DC base bias                  | Bias       |
| R7   | 4.7 k $\Omega$    | Lower voltage divider — DC base bias                  | Bias       |
| R12  | 750 $\Omega$      | Collector load / output impedance                     | RF         |
| R1   | 700 $\Omega$      | Emitter degeneration — stability and gain control     | Bias       |
| R2   | 1 k $\Omega$      | IF output load / spectrum analyser termination        | IF Output  |
| C7   | 5 nF              | RF input AC coupling — blocks DC from source          | RF         |
| C1   | 5 nF              | Collector coupling — passes IF to filter stage        | IF         |
| C2   | 5 nF              | LO emitter coupling — injects LO, blocks DC           | LO         |
| L1   | 1 $\mu$ H         | IF BPF 1st resonator inductor ( $f_0 \approx 12$ MHz) | BPF        |
| C3   | 176 pF            | IF BPF 1st resonator capacitor                        | BPF        |
| L2   | 1 $\mu$ H         | IF BPF 2nd resonator inductor ( $f_0 \approx 20$ MHz) | BPF        |
| C4   | 63.33 pF          | IF BPF 2nd resonator capacitor                        | BPF        |
| XSC1 | —                 | Tektronix virtual oscilloscope (time domain)          | Instrument |
| XSA1 | —                 | Virtual spectrum analyser (frequency domain)          | Instrument |
| XMM2 | —                 | Multimeter — DC operating-point verification          | Instrument |

## DC Bias Point Analysis

### DC Quiescent Point

Voltage divider — Thévenin equivalent:

$$V_{TH} = V_{CC} \cdot \frac{R_7}{R_6 + R_7} = 12 \cdot \frac{4.7}{26.7} \approx 2.11 \text{ V}$$

$$V_E = V_{TH} - V_{BE} \approx 2.11 - 0.7 = 1.41 \text{ V}$$

$$I_E \approx \frac{V_E}{R_1} = \frac{1.41}{700} \approx 2.01 \text{ mA}$$

$$V_C = V_{CC} - I_C R_{12} \approx 12 - 1.51 \approx 10.5 \text{ V}$$

**Q-point:**  $V_{CE} \approx 9.1 \text{ V}$ ,  $I_C \approx 2 \text{ mA}$  — active region confirmed.

### IF Filter Resonance

LC bandpass filter resonant frequency:

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

**Stage 1:**  $L_1 = 1 \mu\text{H}$ ,  $C_3 = 176 \text{ pF}$

$$f_{0,1} = \frac{1}{2\pi\sqrt{10^{-6} \times 176 \times 10^{-12}}} \approx 12.0 \text{ MHz}$$

**Stage 2:**  $L_2 = 1 \mu\text{H}$ ,  $C_4 = 63.33 \text{ pF}$

$$f_{0,2} \approx 20.0 \text{ MHz}$$


Combined topology forms bandpass centred on IF = 8 MHz.

## 3. SIMULATION RESULTS — SPECTRUM ANALYSIS

### Simulation Note


All results obtained via NI Multisim with Tektronix virtual oscilloscope (XSC1) and virtual spectrum analyser (XSA1). Operating condition:  $V_{CC} = 12 \text{ V}$ ,  $f_{RF} = 12 \text{ MHz}$ ,  $f_{LO} = 20 \text{ MHz}$ , two-tone test. Results analysed in both linear amplitude and logarithmic (dB) scale.

RESULT A — Linear Amplitude Scale

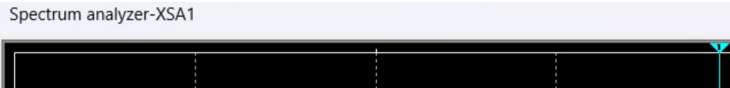

**Description:** Working with amplitude in linear (V or mV) scale. Depending on the result, the sum product ( $f_{LO} + f_{RF} = 32$  MHz) and difference product ( $f_{IF} = 8$  MHz) are visible. In favourable bias conditions both mixing products appear clearly; in other conditions one product dominates. Amplitude linearity calibration is critical for this measurement mode.


RESULT B — Logarithmic (dB) Scale

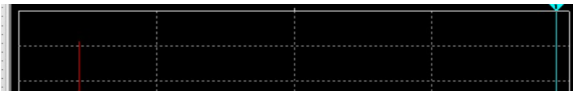

**Description:** With logarithmic (dB) display, unwanted spurious peaks become clearly visible. In some test conditions the undesired IM3 products ( $2f_{LO} - f_{RF} = 28$  MHz and  $2f_{RF} - f_{LO} = 4$  MHz) remain minor; in other bias conditions these undesired peaks rise significantly and are *very clearly visible*, highlighting the critical role of BJT operating-point selection for mixer linearity and spurious suppression.

RESULT C — Experimental Verification (Comprobación)

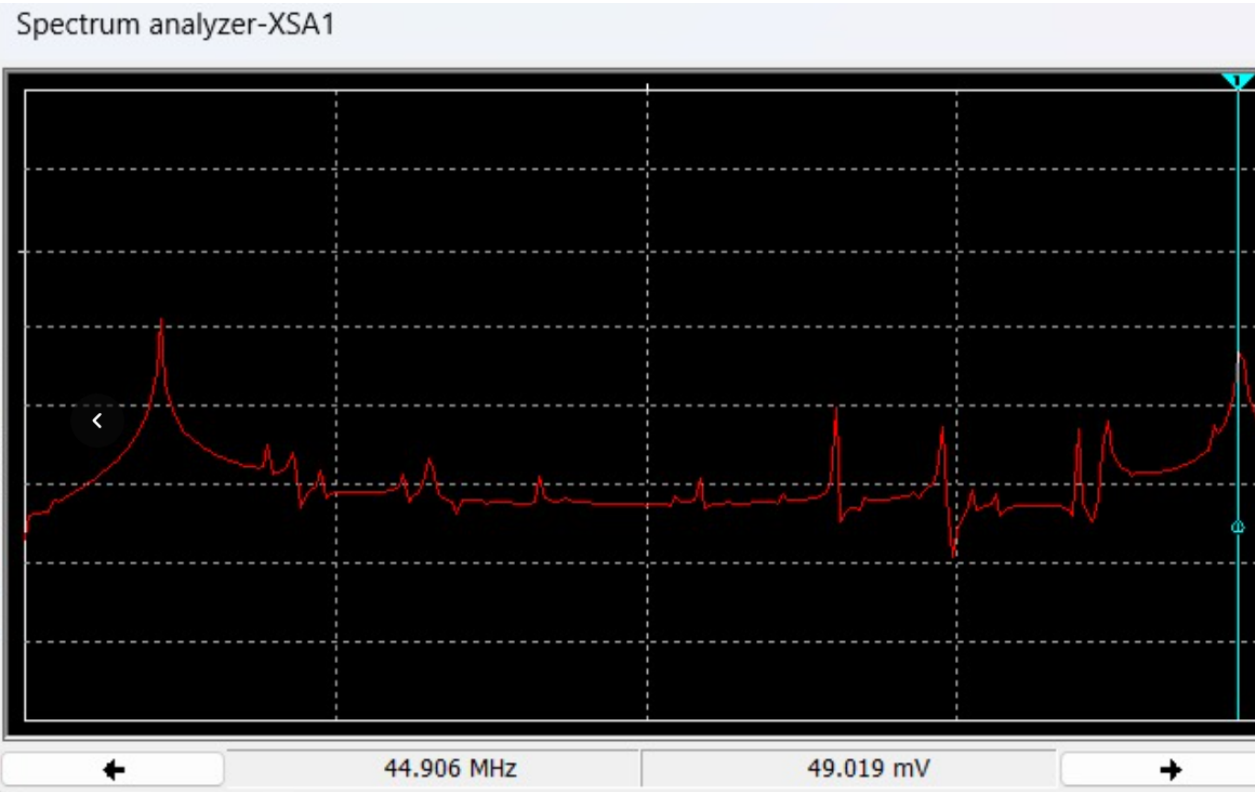Final verification confirming theoretical mixing frequencies.



Verification confirms: IF product at 8 MHz, sum product at 32 MHz, and IM3 products at 4 MHz and 28 MHz — consistent with theoretical prediction from the nonlinear power-series device model. This comprobación validates both the circuit operation and the simulation methodology.

4. ELECTRICAL SPECIFICATIONS

| Parameter                        | Value           | Unit       | Notes                                      |
|----------------------------------|-----------------|------------|--------------------------------------------|
| RF Input Frequency               | 12              | MHz        | V4 — AC sine source                        |
| RF Input Amplitude               | 10              | mVrms      | Small-signal regime                        |
| LO Frequency                     | 20              | MHz        | V2 — emitter injected                      |
| LO Drive Level                   | 50              | mVrms      | $\approx -20$ dBm into $700\ \Omega$       |
| IF Output Frequency              | 8               | MHz        | $f_{IF} =  f_{LO} - f_{RF} $ , wanted      |
| Sum Product                      | 32              | MHz        | Attenuated by IF BPF                       |
| IM3 — Lower                      | 4               | MHz        | $2f_{RF} - f_{LO}$ , spurious              |
| IM3 — Upper                      | 28              | MHz        | $2f_{LO} - f_{RF}$ , spurious              |
| Supply Voltage                   | 12              | V DC       | V1 — BJT bias rail                         |
| Quiescent Collector Current      | $\approx 2$     | mA         | Estimated from bias network                |
| $V_{CE}$ Q-point                 | $\approx 9.1$   | V          | Active region operation                    |
| IF Filter Stage 1 ( $L_1, C_3$ ) | $\approx 12$    | MHz        | $f_0 = 1/2\pi\sqrt{L_1 C_3}$               |
| IF Filter Stage 2 ( $L_2, C_4$ ) | $\approx 20$    | MHz        | $f_0 = 1/2\pi\sqrt{L_2 C_4}$               |
| IF Load Resistance ( $R_2$ )     | 1               | k $\Omega$ | Output / analyser termination              |
| Active Device                    | 2N2222A NPN BJT |            | $h_{FE} \approx 100-300$ , $f_T > 300$ MHz |
| Circuit Topology                 | Common-Emitter  |            | LO at emitter — $g_m$ modulation           |

## 5. NONLINEAR DEVICE MODEL — TAYLOR SERIES ANALYSIS

The BJT 2N2222A collector current as a function of the total AC signal  $v = v_{RF} + v_{LO}$  can be expanded as a Taylor series around the bias point:

$$i_C(v) = a_1 v + a_2 v^2 + a_3 v^3 + a_4 v^4 + \dots$$

- $a_1$  — linear transconductance (small-signal gain) [A/V]
- $a_2$  — 2nd-order: produces IF, DC, and 2nd harmonic [A/V<sup>2</sup>]
- $a_3$  — 3rd-order: produces IM3 distortion [A/V<sup>3</sup>]
- $a_4$  — 4th-order: produces IM4 / even-order products [A/V<sup>4</sup>]

The **IIP3** and **1 dB compression point**:

$$\text{IIP3} = P_{IN} + \frac{\Delta_{dB}}{2}, \quad P_{1dB} \approx \text{IIP3} - 9.6 \text{ dB}$$

Spurious-Free Dynamic Range:

$$\text{SFDR} = \frac{2}{3} (\text{IIP3} - P_{noise}) \quad [\text{dB}]$$

### Complete Frequency Product Chart

#### IM3 Products — Two-Tone Analysis

Input tones:  $f_1 = 12$  MHz,  $f_2 = 20$  MHz

| Product                | Freq.        |
|------------------------|--------------|
| IF: $f_2 - f_1$        | <b>8 MHz</b> |
| Sum: $f_1 + f_2$       | 32 MHz       |
| IM3 low: $2f_1 - f_2$  | 4 MHz        |
| IM3 high: $2f_2 - f_1$ | 28 MHz       |
| 2nd harm. RF: $2f_1$   | 24 MHz       |
| 2nd harm. LO: $2f_2$   | 40 MHz       |

IM3 products *cannot* be filtered if they fall inside the IF passband — they set the SFDR limit.

| $m$ | $n$ | Frequency (MHz)  | Status         | Notes                     |
|-----|-----|------------------|----------------|---------------------------|
| 1   | 1   | $ 12 - 20  = 8$  | <b>WANTED</b>  | IF output — passed by BPF |
| 1   | 1   | $12 + 20 = 32$   | Rejected       | Sum product — filtered    |
| 2   | 1   | $ 24 - 20  = 4$  | Spurious (IM3) | $2f_{RF} - f_{LO}$        |
| 1   | 2   | $ 12 - 40  = 28$ | Spurious (IM3) | $2f_{LO} - f_{RF}$        |
| 2   | 0   | 24               | Harmonic       | 2nd RF harmonic           |
| 0   | 2   | 40               | Harmonic       | 2nd LO harmonic           |
| 3   | 1   | $ 36 - 20  = 16$ | Spurious       | 3rd-order product         |
| 1   | 3   | $ 12 - 60  = 48$ | Spurious       | 3rd-order product         |

## 6. CONVERSION GAIN, NOISE FIGURE & CASCADED CHAIN ANALYSIS

### Conversion Gain

$$G_C = \frac{P_{IF}}{P_{RF}} \quad [\text{dB}]$$

For a BJT resistive mixer in common-emitter topology, the small-signal transconductance at the Q-point:

$$g_m \approx \frac{I_C}{V_T} = \frac{2 \text{ mA}}{26 \text{ mV}} \approx 77 \text{ mS}$$

Active BJT mixers:  $G_C = +5$  to  $+15$  dB.

Passive diode mixers:  $G_C = -6$  to  $-8$  dB.

### Friis Cascaded Noise Figure

$$F_{sys} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots$$

Noise temperature equivalent:

$$T_e = (F - 1) \cdot T_0, \quad T_0 = 290 \text{ K}$$

Example:  $\text{NF} = 6 \text{ dB} \Rightarrow F = 4 \Rightarrow T_e = 870 \text{ K}$ .

The first-stage gain  $G_1$  dominates system NF. A low-NF LNA before the mixer suppresses the mixer's noise contribution by a factor of  $G_1$ .

## S-Parameters & Impedance Matching

| Param.   | Definition                                   |
|----------|----------------------------------------------|
| $S_{11}$ | Input return loss — RF port reflection       |
| $S_{21}$ | Forward conversion gain: RF $\rightarrow$ IF |
| $S_{22}$ | Output return loss — IF port                 |
| $S_{12}$ | Reverse isolation: IF $\rightarrow$ RF       |
| $S_{31}$ | LO-to-RF leakage (feedthrough)               |

### Reflection & VSWR

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$RL = -20 \log |\Gamma| \quad [\text{dB}], \quad VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$P_{dBm} = 10 \log \left( \frac{P_W}{1 \text{ mW}} \right), \quad V_{rms} = \sqrt{P \cdot R}$$

## 7. ENGINEERING NOTES & DESIGN RECOMMENDATIONS

Observations from Simulation

- The wanted IF product at 8 MHz is confirmed in both linear and dB spectrum display modes.
- IM3 products at 4 MHz and 28 MHz are clearly visible in dB view; their amplitude relative to the IF varies with bias point and LO drive level.
- The sum product at 32 MHz is attenuated by the dual-stage LC bandpass filter.
- At unfavourable bias conditions, IM3 peaks become prominently elevated — demonstrating that Q-point optimisation is critical for spurious-free performance.

Recommended Improvements

- Use a double-balanced diode ring mixer for superior even-order spur rejection ( $>25\text{ dBc}$ ) and LO–RF isolation ( $>30\text{ dB}$ ).
- Add a dedicated Chebyshev IF bandpass filter ( $n = 5$ ) to suppress out-of-band IM3 products below noise floor.
- Characterise with a calibrated VNA for IIP3 and  $P_{1\text{dB}}$  using a standard two-tone test.
- For IQ architecture, replace with a Gilbert-cell (MC1496 / SA602) for controlled conversion gain and balanced port impedances.

Measurement Disclaimer

All numerical values are derived from NI Multisim simulation. For professional validation, use a calibrated VNA with full 2-port SOLT calibration and a real-time spectrum analyser with at least 70 dB dynamic range. Recommended instruments: Keysight E5063A VNA, Rohde & Schwarz FSW Spectrum Analyser.